

# Practical 3


## Functionality

English


A User interface that is capable of analysing a set count of numerical inputs. When all the numbers are input, the sequence is checked against an expected sequence, and if it passes - an output pin is enabled. Otherwise, an error is indicated, and the sequence resets.

## Diagrams

### State Diagram

 

### FSM Diagram

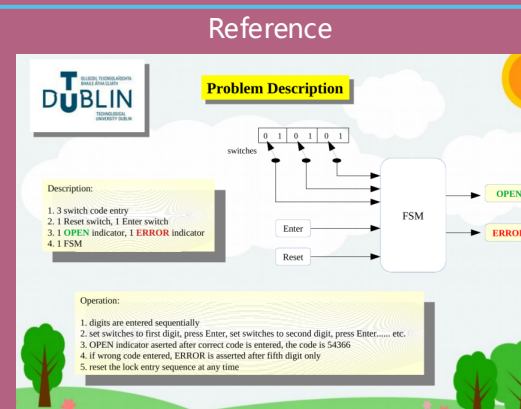

### State Transition Diagram

Description	Current State	Inputs	RESET	ENTER	Next State	Signal	Output
RESET	ANY	x x x x	1	RISE UP	S0	Set to 0	Set to 0
INPUT DIGIT 1 PASS	S0	1 0 1 0	0	RISE UP	S1	Set to 1	Set to 1
INPUT DIGIT 1 FAIL	S0	1 1 1 0	0	RISE UP	S2	Set to 1	Set to 1
INPUT DIGIT 2 PASS	S1	1 0 1 0	0	RISE UP	S2	Set to 1	Set to 1
INPUT DIGIT 2 FAIL	S1	1 1 1 0	0	RISE UP	S2	Set to 1	Set to 1
INPUT DIGIT 3 PASS	S2	0 1 1 0	0	RISE UP	S3	Set to 1	Set to 1
INPUT DIGIT 3 FAIL	S2	1 0 1 1	0	RISE UP	S3	Set to 1	Set to 1
INPUT DIGIT 4 PASS	S3	1 1 1 0	0	RISE UP	S4	Set to 1	Set to 1
INPUT DIGIT 4 FAIL	S3	1 1 1 1	0	RISE UP	S4	Set to 1	Set to 1
INPUT DIGIT 5 PASS	S4	1 1 1 1	0	RISE UP	S5	Set to 1	Set to 1
INPUT DIGIT 5 FAIL	S4	1 1 1 1	0	RISE UP	S0	Set to 0	Set to 0
RESET IN 5 SECONDS	S5	x x x x	0	x	S0	Set to 0	Set to 0

### Circuit Components

### D flip-flop

### State count

3 bits

### ripple counter

mod 6

6 States

### Boolean Failed

1 bit

true/false

### Encoded State Transition Diagram

Todo

## Derive Logic expressions

## Draw the circuit diagram

## Write the VHDL for the components to be used (if not lib)

## Write the VHDL code (structural style) for the FSM

## Test/verify the operation (simulator)

## Document

## Generate presentation/report